
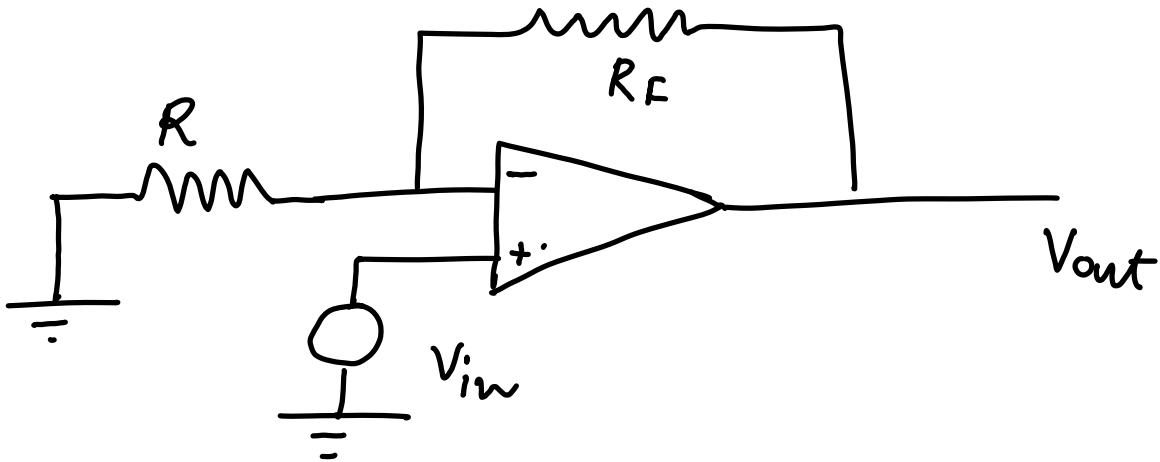


② Non-inverting amplifier

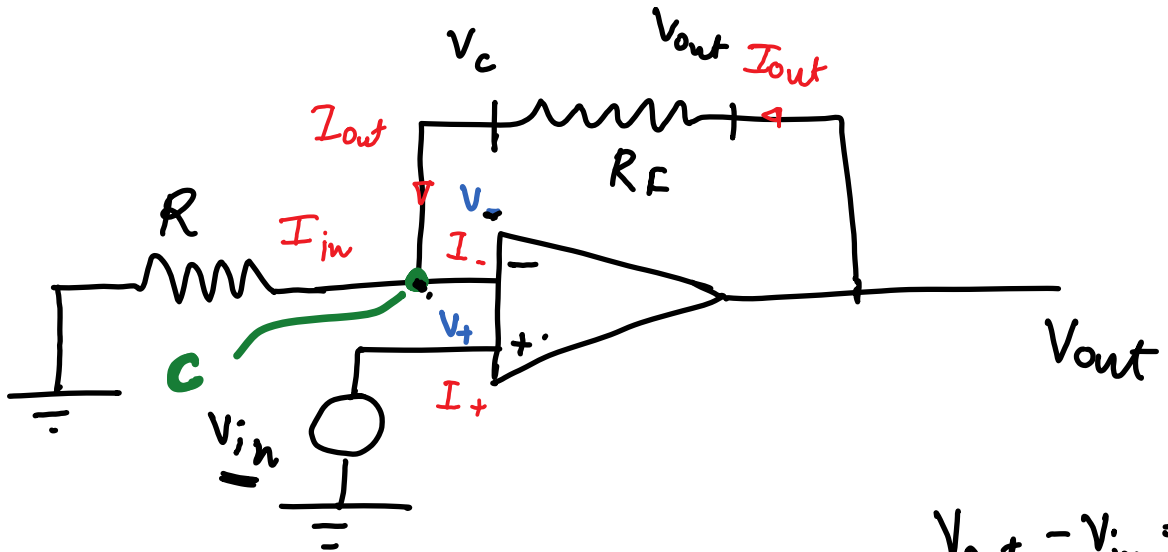


Compute  $\frac{V_{out}}{V_{in}} = ?$



$$V_{out} - V_c = I_{out} R_F \quad \longrightarrow \quad V_{out} - V_{in} = I_{out} R_F$$
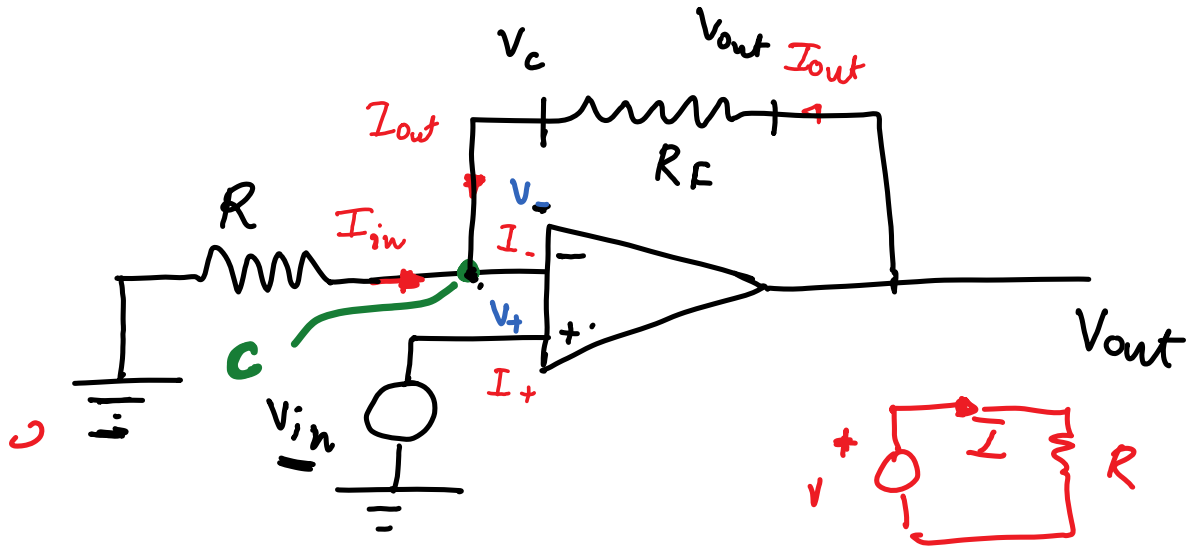
$$\left\{ \begin{array}{l} V_{in} = V_+ \\ V_+ = V_- \\ V_c = V_- \end{array} \right. \quad (\text{op-amp assumption}) \quad \left. \vphantom{\left\{ \right.} \right\} \begin{array}{l} \uparrow \\ V_{in} = V_c \\ \underline{\underline{\quad}} \end{array}$$



① —  $V_{out} - V_{in} = I_{out} R_f$  (from previous page)

At c :  $I_{out} + I_{in} = I_- = 0$

op-amp assumption

② —  $I_{out} = -I_{in}$

$V_{in}$  is in parallel with the input resistor  $R$ .

③ —  $V_c - 0 = -I_{in} R$

Because  $I_{in}$  is assumed to flow from 0 to c

from ①  $\frac{V_{out} - V_{in}}{R_f} = I_{out}$  ||  $-\frac{V_{in}}{R} = I_{in}$  from ③

From ③  $\frac{V_{out} - V_{in}}{R_f} = \frac{V_{in}}{R}$

$$\frac{V_{out} - V_{in}}{R_f} = \frac{V_{in}}{R}$$

$$\frac{V_{out}}{R_f} = V_{in} \left[ \frac{1}{R_f} + \frac{1}{R} \right]$$

$$\frac{V_{out}}{V_{in}} = \left( 1 + \frac{R_f}{R} \right)$$


- ①  $V_{out} \propto V_{in}$  (non-inverting)
- ② amplification  $1 + \frac{R_f}{R}$
- ③ let  $\underline{R} \gg \underline{R_f}$

$$\frac{V_{out}}{V_{in}} \approx 1 \quad \Rightarrow \quad V_{out} \approx V_{in}$$

**BUFFER or  
FOLLOWER**


helps to isolate the  
voltage source ( $V_{in}$ ) because  
of the high resistance  $R \rightarrow \infty$

### ③ Differentiator

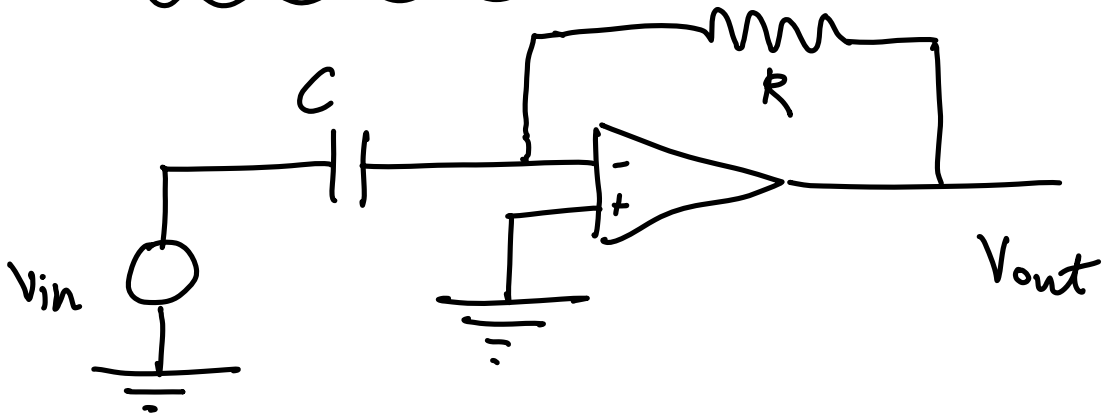

$$V_{out} = f(V_{in})$$

↑  
derivative

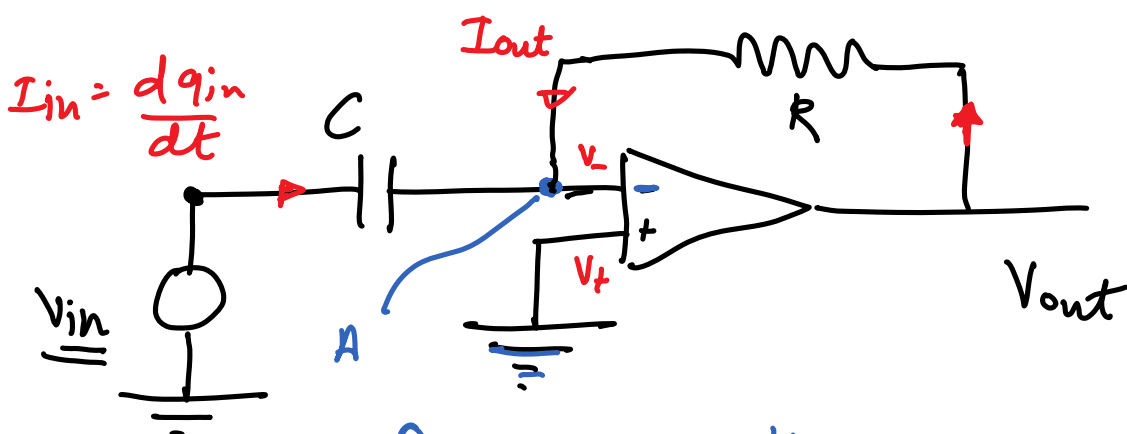

$$V_{out} - V_A = I_{out} R$$

$$V_{in} - V_A = \frac{q_{in}}{C}$$

At A:

$$I_{out} + I_{in} = I_- = 0$$

$$\left. \begin{array}{l} V_- = V_+ = 0 \\ V_A = V_- \end{array} \right\} V_A = 0$$

$$\begin{aligned} \textcircled{1} \quad V_{out} - V_A &= \underline{I_{out}} R \\ \textcircled{2} \quad V_{in} - V_A &= \frac{q_{in}}{C} \end{aligned} \quad \left. \begin{array}{l} \text{At A:} \\ I_{out} + I_{in} = I_- = 0 \end{array} \right\}$$

$$\underline{I_{out}} = -I_{in} = -\frac{dq_{in}}{dt}$$


From  $\textcircled{1}$  &  $\textcircled{2}$

$$\frac{V_{out}}{R} = -\frac{d}{dt} (C V_{in})$$

$$\frac{V_{out}}{R} = -C \frac{dV_{in}}{dt}$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$


## ④ Integrator

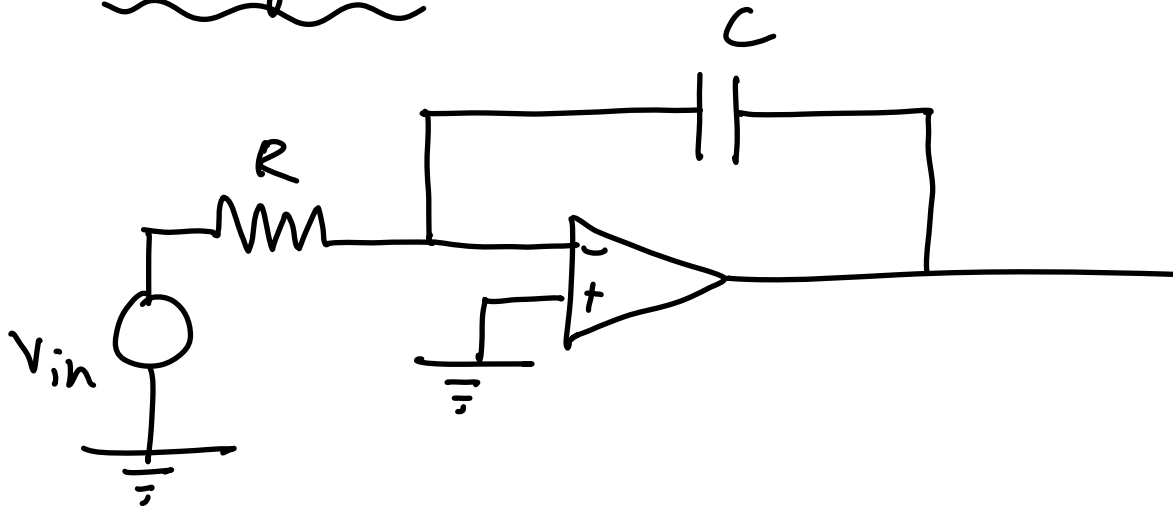

Show that


$$V_{out} = -\frac{1}{RC} \int_0^t V_{in}(\tau) d\tau$$

⑤ Summer

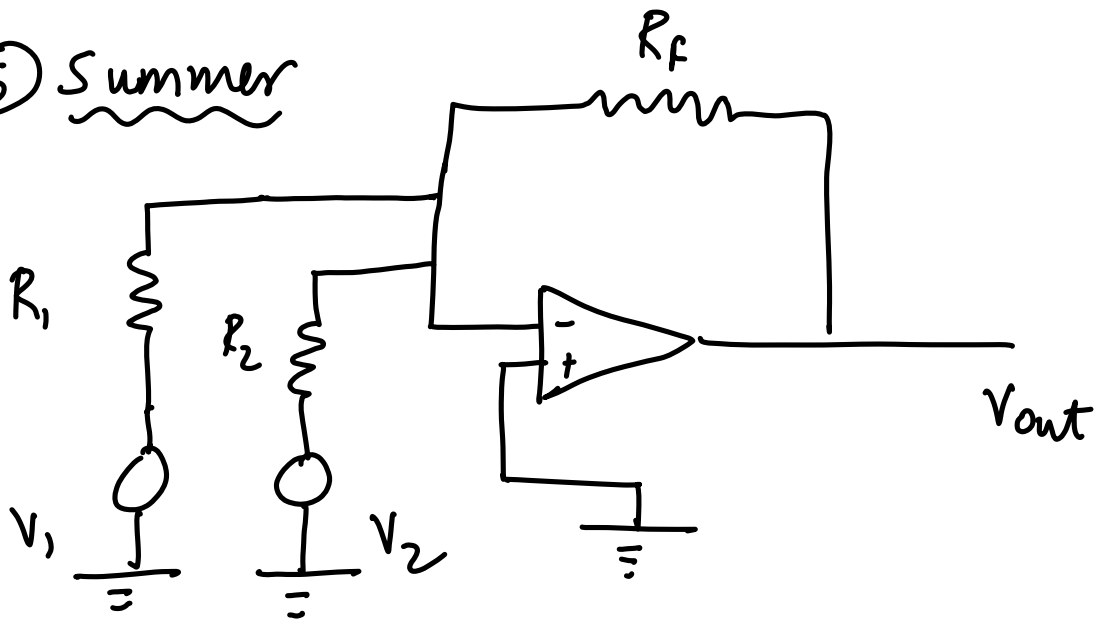

Compute  $V_{out}$  as a function of  $V_1, V_2$

---

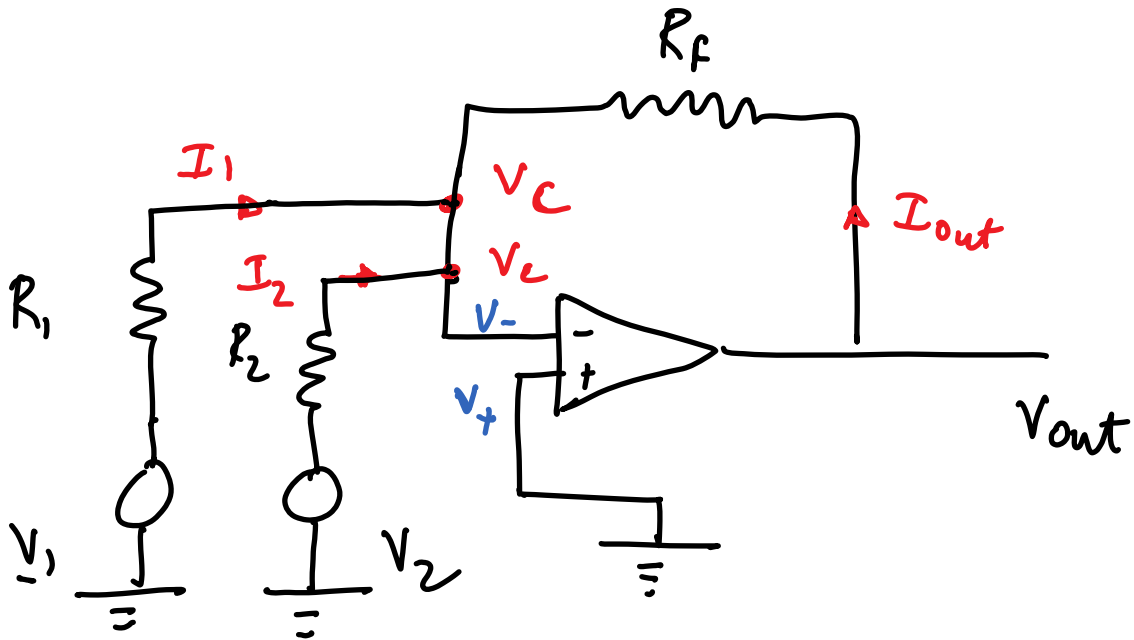

$$\left. \begin{aligned} V_{out} - V_c &= I_{out} R_f \\ V_1 - V_c &= I_1 R_1 \\ V_2 - V_c &= I_2 R_2 \end{aligned} \right\} \begin{array}{l} \text{Unknowns } I_{out}, I_1, I_2 \\ V_c, V_{out} \end{array}$$

$$\left. \begin{aligned} V_+ &= V_- \\ V_c &= V_- \\ V_+ &= 0 \end{aligned} \right\} V_+ = V_- = V_c = 0$$

$$I_{out} + I_1 + I_2 = I_- = 0$$

$$\frac{V_{out}}{R_f} + \frac{V_1}{R_1} + \frac{V_2}{R_2} = 0$$

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$



$$R_1 = R_2 = R$$

$$V_{out} = -\frac{R_F}{R} (V_1 + V_2)$$